

## Load Calculations - Branch and Feeder Circuits Review

Magic numbers: 125%, 80%, 3VA, 175%, 250%, 1.732, 115%, 140%, 12.9, 21.1

### Read NEC 110.14(C)

#### Volt Amps, or VA

Amps X Volt = VA (Volt Amperes, Single Phase),  $35 \times 230 = 8050 \text{ VA}$

Amps X Volt X 1.732 = (Volt Amperes, 3 Phase),  $35 \times 480 \times 1.732 = 29,098 \text{ VA}$

#### Min Circuit Size (Read NEC 210.19 and 210.20A)

Amps X 1.25 = Amps X 125% =  $25\text{A} \times 1.25 = 31.25\text{A}$

#### Max Continuous Load

Amps X 0.80 = Amps X 80% =  $75\text{A} \times 0.80 = 60\text{A}$

### NEC Table 310.15(B)(16)

#### Temperature Derating (See NEC Table 310.15(B)(2)(a))

#### Adjustment Factors for more than 3 current carrying conductors (See NEC Table 310.15(B)(3)(a))

Amps X 0.70 = Amps X 70% =  $80\text{A} \times 0.70 = 56\text{A}$

Amps / 0.70 = Amps / 70% =  $80 / 0.70 = 114\text{A}$

#### Voltage Drop

Constant for copper = 12.9

Constant for aluminum = 21.2

$VD = 2 \times K \times I \times L / CM$

$VD = 1.732 \times K \times I \times L / CM$

<http://www.risingedgeservices.com/voltageDrop.html>

#### Motor Calculations

FLC X 125% = MCA (Min. Circuit Ampacity)

Round

Temp Adjustment

Number of Wires Adjustment

$MCA / (\text{Temp Adjustment} \times \text{Number of Wires Adjustment}) = \text{MCA after Adjustments}$

Check your termination temps

Choose your conductors

#### Branch Circuit Ampacity

Single Phase =  $VA / V = \text{Amps}$

$$3 \text{ Phase} = VA / (V \times 1.732)$$

What's the ampacity of three, 5.6 kW, 3 phase, 480VAC, immersion heaters?

What's the Min. Circuit Ampacity?

$$(5.6 \times 1000) / (480 \times 1.732) = 6.74A$$

$$6.74A \times 3 \text{ fixtures} = 20.22A$$

$$20.22A \times 1.25 = 25A$$

### Lighting Loads

What's the minimum lighting load for a 4,200 sq/ft home?

$$4200 \times 3VA = 12600W = 12600W/240VAC = 52.5A$$

What's the minimum lighting load for a 30,000 sq/ft armory?

$$30000 \times 1VA = 30,000VA = 30,000 / (480 * 1.732) = 36A$$

How many 250 watt lighting fixtures, with a power factor of 90%, can be placed on a 20A, 277V, lighting circuit?

$$20A \times 0.80 = \text{Max amps on a 20 amp circuit (Due to continuous loading)} = 16A$$

$$250W / 0.90 = 278W$$

$$278W / 277V = 1A \text{ per fixture}$$

This make math easy. If each fixture take 1A, then you can put 16 fixtures on the circuit.

### Practical Application #3

You are an electrician installing the wiring in a new home. The homeowner desires that a ceiling fan with light kits be installed in five different rooms. Each fan contains a light kit that can accommodate four 60 watt lamps. Each fan motor draws a current of 1.8 amps when operated on high speed.

It is assumed that each fan can operate more than three hours at a time. The fans are to be connected to a 15 amp circuit. How many fans can be connected to the 15 amp circuit? How many circuits will be required to supply power to all the fans?

$$(4 \times 60) / 120 = 2A = \text{Lighting load on each circuit.}$$

$$1.8A = \text{motor load on each circuit.}$$

$$2A + 1.8A = 3.8A = \text{Total load for each fan and light kit.}$$

$$15 \times 0.80 = \text{Max amps on a 15 amp circuit (Due to continuous loading)} = 12A$$

$12A / 3.8A = 3.16$  fans on each circuit? No, only 3 fans can go on the circuit.

$19A / 12A = 1.58$  Circuits are needed to power all the fans and light kits.

#### **Practical Application #4**

A homeowner is installing a swimming pool. You have been asked to install a circuit to operate a 600 watt underwater light and a circulating pump. The motor nameplate reveals that the pump has a current draw of 8.5 amps. The devices are considered continuous duty. Can the power to operate these devices be supplied by a single 20 amp circuit?

$$600W / 120VAC = 5A$$

$$\text{Motor Amps} = 8.5A$$

$$\text{Total Amps} = 5A + 8.5A = 13.5A$$

$$\text{Total Amps} \times 1.25 = 16.88 = 17A$$

$$20A \times 0.80 = \text{Max amps on a 20 amp circuit (Due to continuous loading)} = 16A$$

So, you can connect all that to the 20A circuit. 17A is greater than the 16A continuous load allowed on on 20A circuit.

NEC 110.3

NEC 430.51

NEC 430.122(A) and (B)

#### **Motor Application**

Design the installation of a 230VAC, 15HP, 3 Phase Motor, running a water pump for a commercial cooling system. The motor and pump will be installed 520' from the control panel. The conduit passes through a room where they are using hydrochloric acid as part of the water treatment system. The owner asked that you use XHHW conductors, since that is what is being used on site. The owner also wants the motor to be protected by current limiting time delay fuses, since she is considering adding a Danfoss 15HP FC-302 VFD in the future. Assume 75C connections.

$$15HP \text{ FLC} = 42A$$

$$42A \times 1.25 = 52.5A = \#6 \text{ AWG, CU}$$

$$42A \times 1.75 = 73.5A = 80A \text{ Fuse}$$

$$HP \times 0.7457 \text{ kW} = 15HP \times 0.7457 = 11.19 \text{ kW} = 11 \text{ kW}$$

$$15HP \text{ FC-302 VFD continuous load} = \text{See page 59 in the FC-302 Manual} = 46.2A$$

$$46.2 \times 1.25 = 57.75A = \#6 \text{ AWG, CU}$$

$$46.2 \times 1.75 = 80.85 = 90A \text{ Fuse}$$

What size fused disconnect do you need? 100A

$$VD = (1.732 \times K \times I \times L) / C_{mils} = (1.732 \times 12.9 \times 46.2 \times 520) / 26240 = 20.46 \text{ VD}$$

$$VD / \text{Voltage} = \%VD = 20.46 / 230 = 8.9\% \text{ VD} = \text{Too much \%VD!}$$

$$CM = (1.732 \times K \times I \times D) / VD = (1.732 \times 12.9 \times 46.2 \times 520) / (230 \times 0.05) = 46675 \text{ Cmils} = \#3 \text{ AWG}$$